

Synthesized Driver for Beacons with WSJT Data

Andy Talbot G4JNT

October 2012

The driver is intended as a versatile source adaptable to all VHF and UHF amateur band beacons transmitting frequency agile data modes such as ISCAT, JT65 and JT4. The hardware is based around an LMX2470 Fractional-N synthesizer, updated in real time from a PIC controller. This, in turn, takes in timing information delivered from an external NMEA data source, and optional 1 PPS signal for enhanced accuracy. The synthesizer chip requires an external reference signal, typically at 10MHz. Both signals can come from a GPSDO reference

As the synth chip can only work over the range 500 – 2600MHz, the output is divided down for lower bands, typically by 8 times although higher or lower values are possible.

The unit as supplied for GB3WGI is made up of three modules:

- An LMX2470 development module, modified to remove and bypass its own PIC controller (See http://www.g4jnt.com/LMX2470_DevModule.pdf)
- A PCB carrying the VCO, divider and driver amplifier
- A PCB carrying a PIC for controlling the synth chip
- A LM7808 8V regulator supplying Vin to all three PCBs.

The circuit diagrams for each module and a photo of the complete assembly are shown below.

VCO/Divider Module (Lower right of Photograph)

The packaged VCO runs at approximately 1156MHz. An attenuated output at this frequency is fed back to the PLL module at a level of -5dBm. The VCO also supplies a PE3513 divide by 8 chip. This will function with up to 1.5GHz maximum input frequency. The divider requires 3.0V supply rail which comes from a dedicated LM317L regulator.

The divider output feeds an SGA6289 broadband amplifier MMIC which in turn drives a BFG591 output transistor for a maximum output power (from a 12.0V supply) in the region of 600mW. For the application here, an 8V regulator (not shown in the diagrams) is installed for the entire driver module. At this Vcc the final stage can deliver around 400mW maximum. A preset resistor in the emitter of the BFG591 allows the output level to be reduced to less than +10dBm

Code Generator (Top centre of the Photograph)

A 16F627A PIC takes in the NMEA timing data and 1PPS signal and determines the correct start point for each part of the message transmitted. Depending on the data type, the synthesizer is programmed in real time over its SPI interface. An external key line is provided for ON-OFF keying a PA stage via a separate modulator. The polarity is ground to Tx, open-circuit for space.

Reprogramming the PIC

Table 1 shows the relevant part of the PIC code containing frequency and message data. This is all stored in EE memory, and with care, can be updated by reprogramming this part of the chip only. Note, the CW message can be a variable length field and MUST have the NULL Terminator. The variable length option means it must occupy the last position in the EE data. Be very careful when editing EE data not to accidentally add extra bytes in the preceding sections

To change message data only, the two sections highlighted in red are applicable. The CW message is self explanatory and must be in upper case; note the null terminator. The include file *jt65symb.inc* (or any other file name you may choose) has to be generated using the utility *GENJT65.EXE* contained in <http://www.g4jnt.com/JT65CODE.ZIP> Note this calls up *JT65CODE.EXE* written by K1JT, also included in the .ZIP archive, so make sure both are saved in the same subdirectory)

To change the frequency is a more complex procedure. Consult the data sheet for the LMX2470 to work out the values of N, F and D needed. Two sets of values will be required. One for a frequency grid for JT65 and one for a grid with nice round numbers of Hz to set the carrier frequency accurately.

Only Reg0, Reg1 and Reg7 carry frequency and grid information, highlighted in green in the listing below. The other registers must not be touched as they control PLL configuration information and are only programmed into the chip once at startup.

Note that in the listing shown, there are two possible values for Reg 0 (containing the 12 LSBs of the frequency setting) – one of which is remmed out. ONE of these lines MUST ALWAYS be remmed out – only a single Reg0 value must be used! The two possible values correspond to the desired JT65 reference or sync tone when the receiver is tuned to place the nominated carrier frequency (defined by the other grid) to either 800Hz or 1500Hz

The sync tone must always be delivered to the receiver at 1270.46Hz (subject to the 5.38Hz grid setting accuracy).

For a 1500Hz tuning point, the sync tone must fall at $F_{\text{carrier}} - 1500 + 1270.46\text{Hz}$.

For 800Hz tuning tone, the sync has to be placed at $F_{\text{carrier}} - 800 + 1270.46\text{Hz}$.

```

ConfigData      ;24 bit words sent in sequence for registers that remain unchanged
; Fout 1155.894164MHz Resolution 43.066406Hz
; R = 1      D = 232199      N = 115      F = 136862
de 0x41, 0xB0, 0x71 ; Reg1 R + D (LSBs)
de 0xC0, 0x07, 0x43 ; Reg2 IF Disabled
de 0x20, 0x00, 0x15 ; Reg3 Charge Pump Current
de 0xBC, 0x2B, 0xC7 ; Reg4 Timeout / FastLock
de 0x10, 0x1F, 0x49 ; Reg5 IF not used
de 0x00, 0xC4, 0x4B ; Reg6 Config and setup bits
de 0x0E, 0x02, 0x1D ; Reg7 D(MSBs) + F (MSBs)
de 0x00, 0x08, 0x6F ; Reg8 Dither settings
EndConfigData


; Fout 1155.894164MHz Resolution 43.066406Hz (11025/2048 * 8)
; R = 1      D = 232199      N = 115      F = 136862
JTFFreqData    ;Registers affecting freq and grid for JT65 sequence
; de 0x0E, 0x6D, 0x3C ; Reg0 N + F (LSBs JT65 sync for 1500Hz reference tone)
de 0x0E, 0x6E, 0x40 ; Reg0 N + F (LSBs ditto for 800Hz reference tone)
de 0x41, 0xB0, 0x71 ; Reg1 R + D (LSBs)
de 0x0E, 0x02, 0x1D ; Reg7 D(MSBs) + F (MSBs)
EndJTFFreqData

; Fout 1155.896MHz Resolution 40Hz /8 = 144.487
; R = 1      D = 250000      N = 115      F = 147400
CarrierFreqData ;Registers affecting freq and grid for exact freq setting
de 0x0E, 0x7F, 0x90 ; Reg0 N + F (LSBs)
de 0x41, 0x09, 0x01 ; Reg1 R + D (LSBs)
de 0x0F, 0x42, 0x3D ; Reg7 D(MSBs) + F (MSBs)
EndCarrierFreqData

JT65MsgData
include "jt65symb.inc" ;JT65 tones


CWMsg
de "GB3WGI IO64BL",0

```

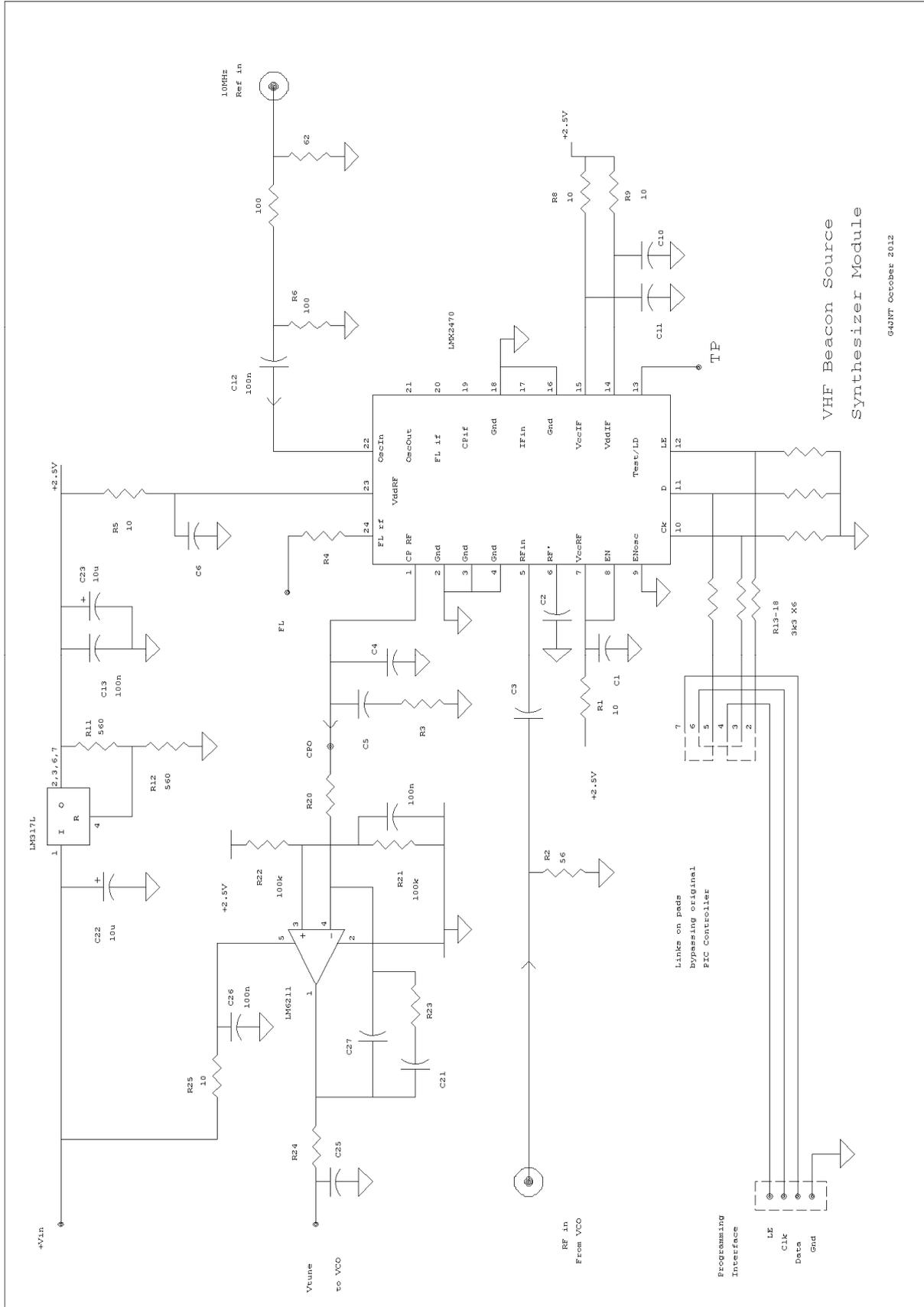VHF Beacon Source
Synthesizer Module



GAUNT October 2012

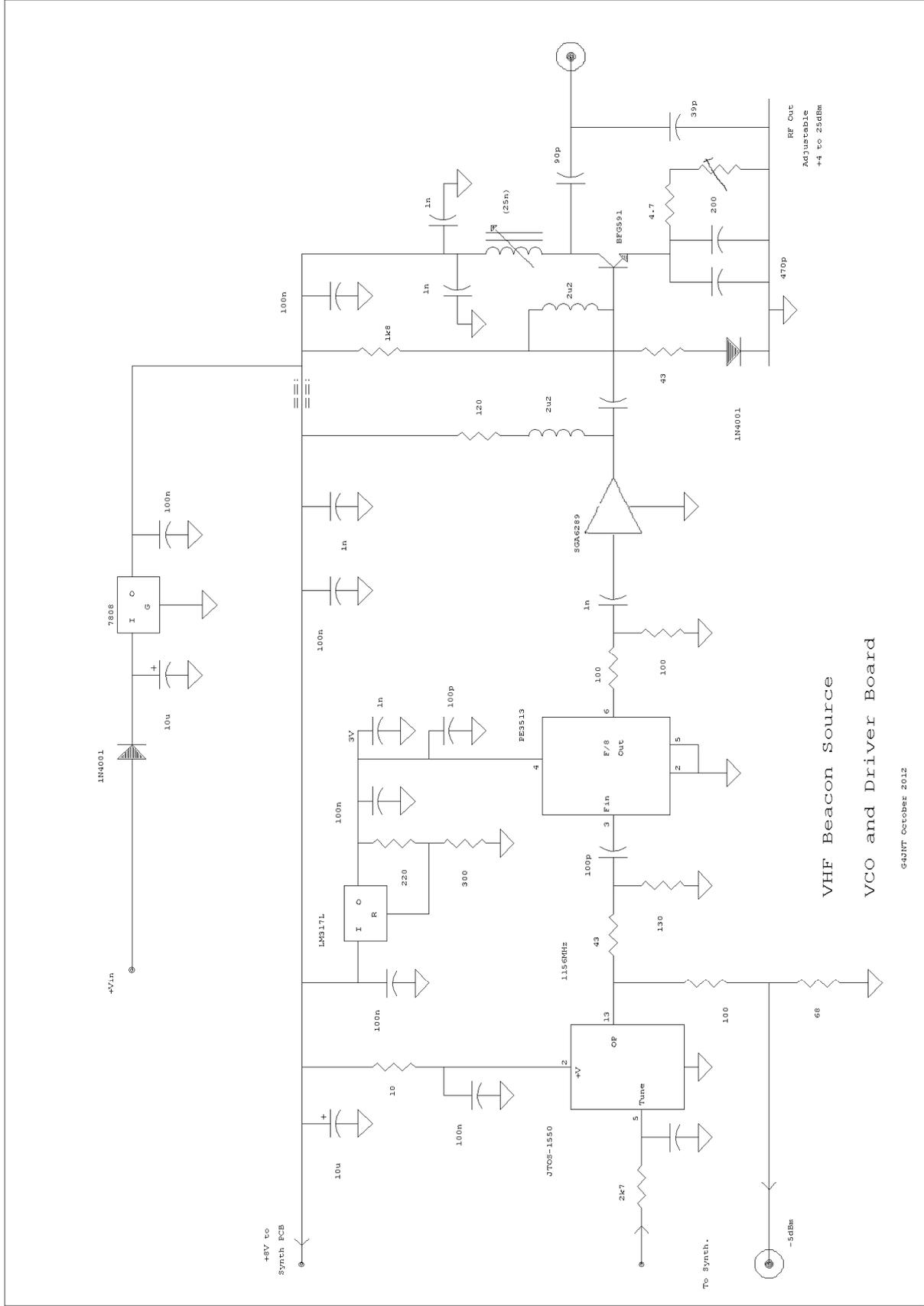



VHF Beacon Source
VCO and Driver Board

640JNT October 2012

Output Spectrum Plain Carrier

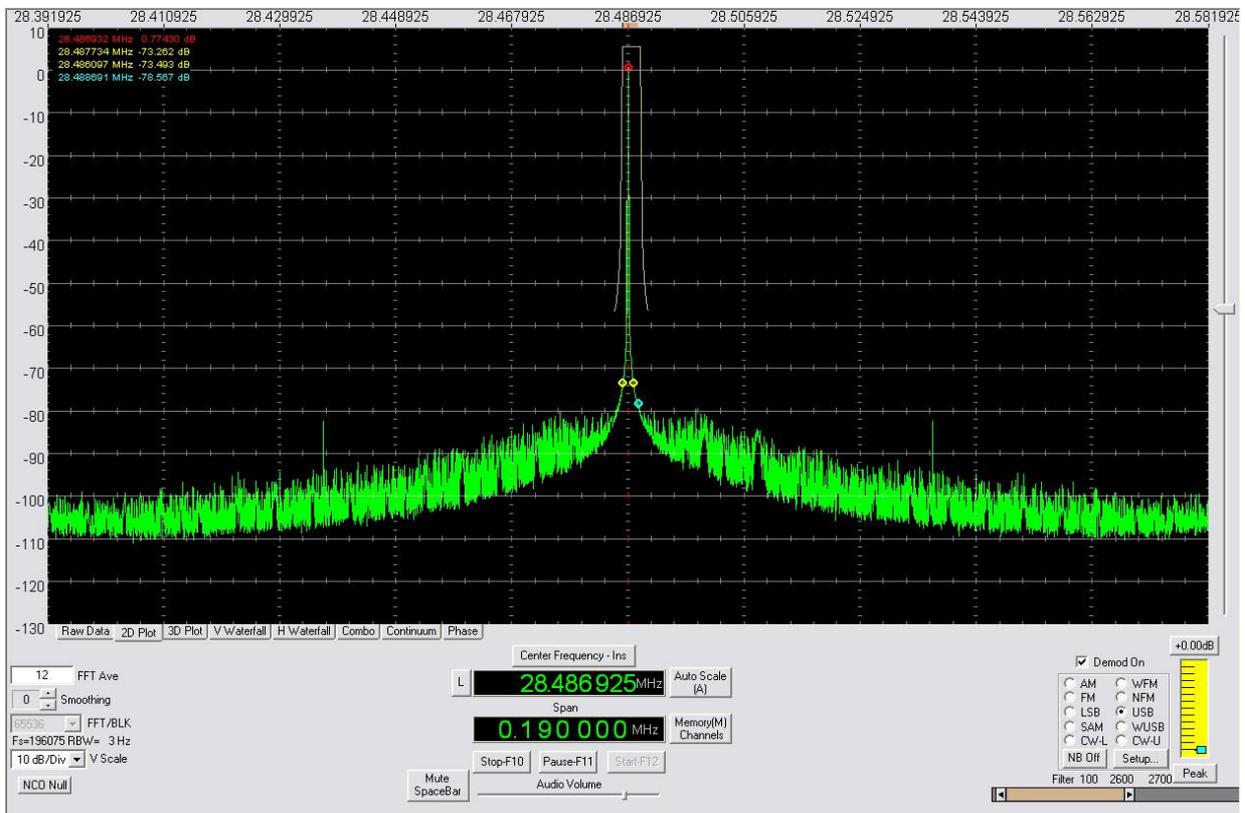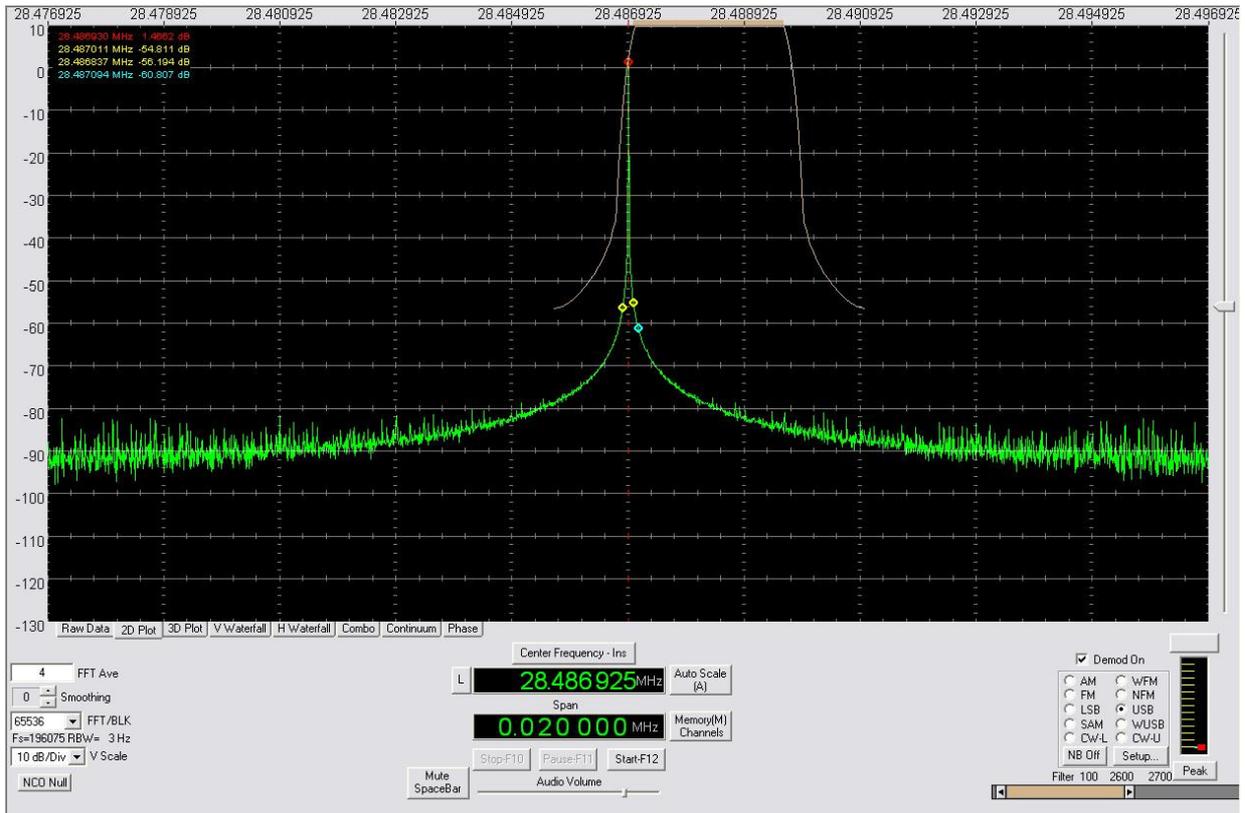


Output Spectrum During JT65 sequence

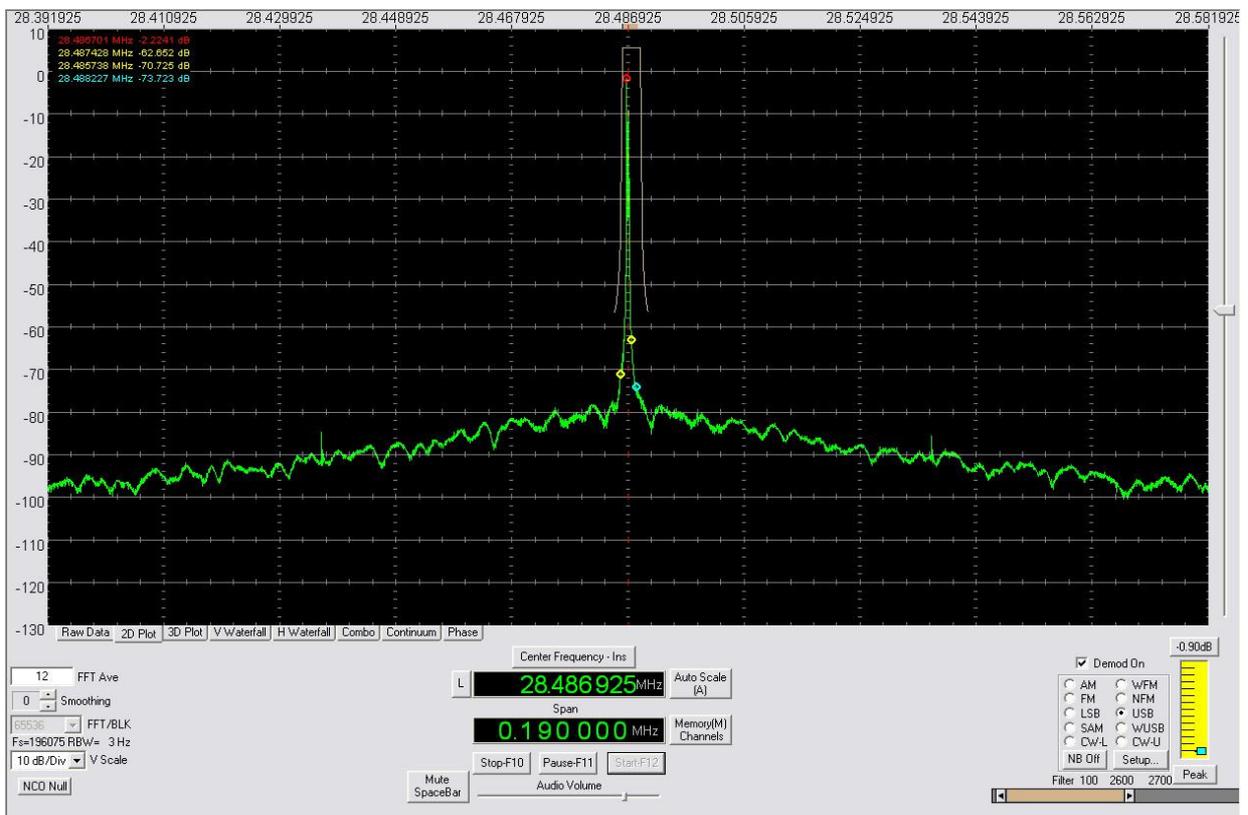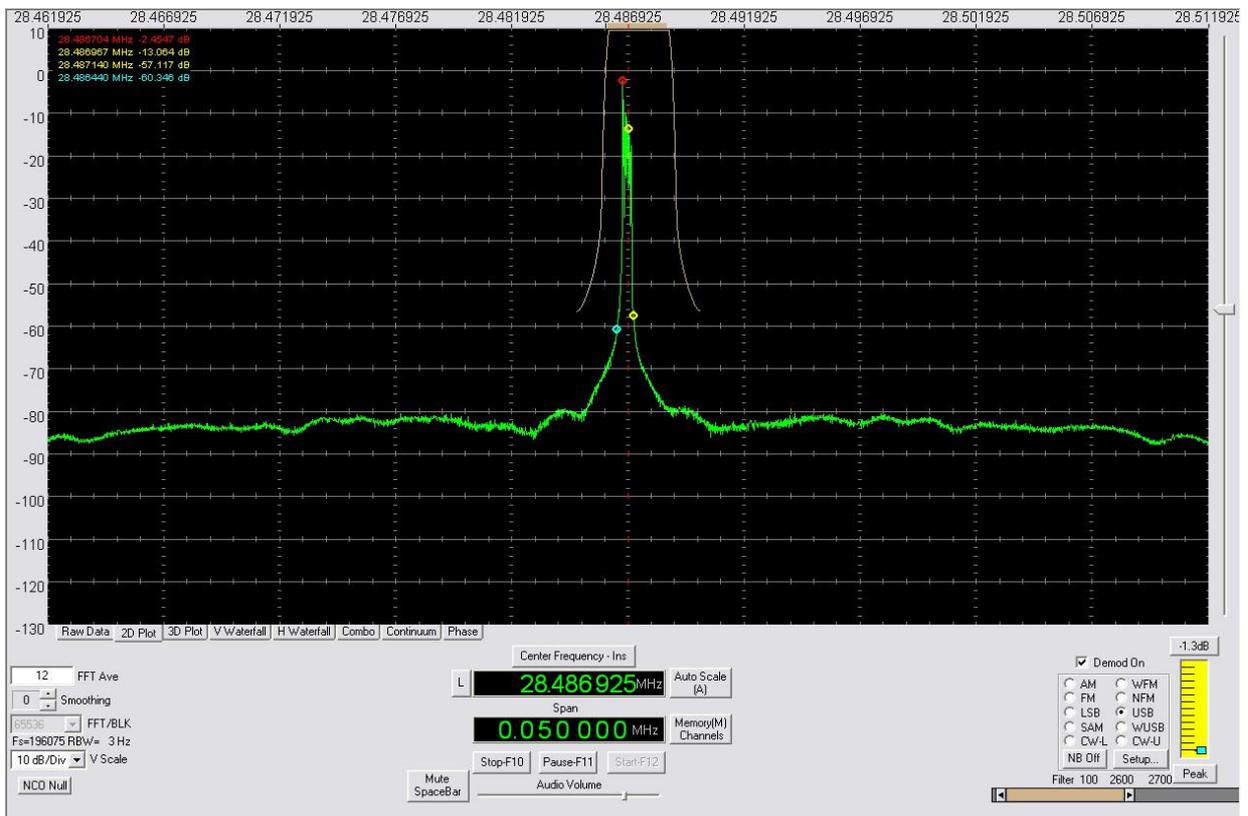

Appendix A


RF Source PCB Layout

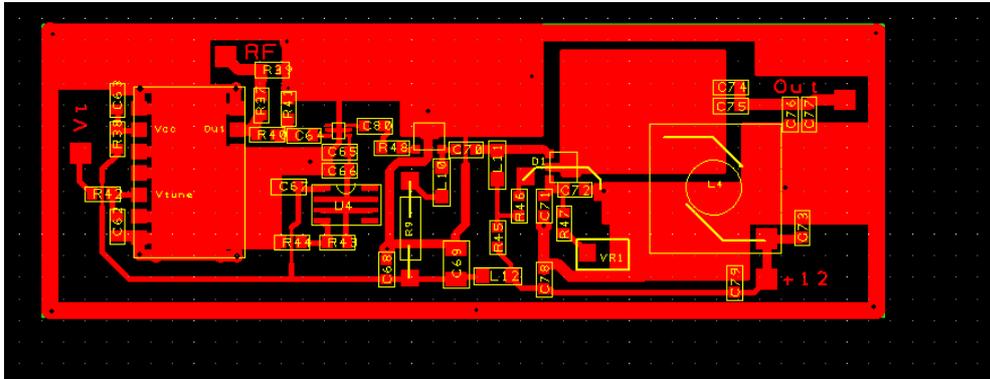

Copper layouts at 1:1 Scale for direct printing to acetate or Press-N-Peel

144BcnSrc_CopperMirror1.pdf and 144BcnSrc_Copper1.pdf

PIC Code Generator PCB Layout

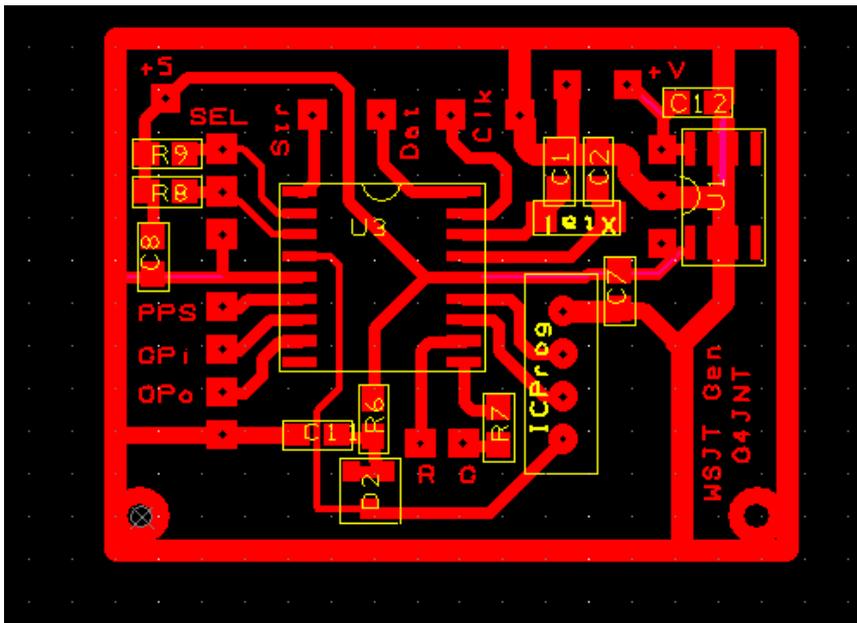

Copper layouts at 1:1 Scale for direct printing to acetate or Press-N-Peel

WSJTGEN_PCBMirror1.pdf and WSJTGEN_PCB1.pdf

(nb. The FET controlling the external On-Off keying is not included on this PCB layout)

PCB Layouts in .PDF Format http://www.g4jnt.com/144_Driver_PCBs.zip

LMX2470 Synthesizer Module

